


# Lecture 3/

	Properties	Time Domain	Laplace Transform
1	Linearity	$a_1x_1(t) + a_2x_2(t) + \dots + a_nx_n(t)$	$a_1X_1(s) + a_2X_2(s) + \dots + a_nX_n(s)$
2	Frequency Shifting	$e^{-\alpha}x(t)$	$F(s + \alpha)$
3	Time Delay	$x(t - a)u(t - a)$	$e^{-\alpha}X(s)$
4	Time Scaling	$x(\alpha t)$	$\frac{1}{\alpha}X\left(\frac{s}{\alpha}\right)$
5	Time Differentiation	$\frac{d}{dt}x(t)$	$sX(s) - x(0^-)$
6	Time Integration	$\int_{-\infty}^t x(\tau)d\tau$	$\frac{X(s)}{s} + \frac{1}{s} \int_{-\infty}^{0^-} x(\tau)d\tau$
7	<del>Initial Value Theorem</del>	<del><math>\lim_{t \rightarrow 0^+} x(t)</math></del>	<del><math>\lim_{s \rightarrow \infty} sX(s) = x(0^+)</math></del> <span style="float: right;">✗</span>
8	<del>Final Value Theorem</del>	<del><math>\lim_{t \rightarrow \infty} x(t)</math></del>	<del><math>\lim_{s \rightarrow 0} sY(s) = x(\infty)</math></del> <span style="float: right;">✗</span>
9	Time Convolution	$x(t) * y(t)$	$X(s)Y(s)$

Signal	Laplace Transform
1. $\delta^{(n)}(t)$	$s^n$
2. 1 or $u(t)$	$\frac{1}{s}$
3. $\frac{t^n \exp(-\alpha t)u(t)}{n!}$	$\frac{1}{(s + \alpha)^{n+1}}$
4. $\cos \omega_0 t u(t)$	$\frac{s}{s^2 + \omega_0^2}$
5. $\sin \omega_0 t u(t)$	$\frac{\omega_0}{s^2 + \omega_0^2}$
6. $\exp(-\alpha t) \cos \omega_0 t u(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_0^2}$
7. $\exp(-\alpha t) \sin \omega_0 t u(t)$	$\frac{\omega_0}{(s + \alpha)^2 + \omega_0^2}$

Today

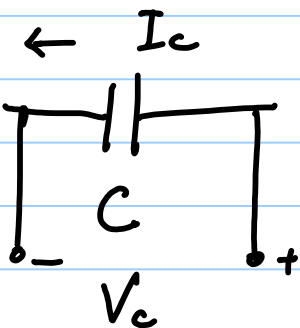- Laplace models for capacitor & inductor
- example
- properties of LT
- Inverse Laplace Transform




$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$\downarrow \mathcal{L}$

$$\begin{aligned} \underline{I_c(s)} &= C \left[ sV_c(s) - v_c(0^-) \right] \\ &= Cs \underline{V_c(s)} - C v_c(0^-) \end{aligned}$$


If  $v_c(0^-) = 0$  (zero IC)
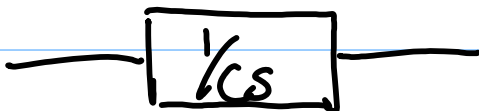
$$\begin{aligned} I_c(s) &= Cs V_c(s) \\ \Rightarrow \frac{V_c(s)}{I_c(s)} &= \frac{1}{Cs} \leftarrow \text{looks like a "resistor"} \\ &\text{Complex Impedance} \end{aligned}$$



If  $v_c(0^-) \neq 0$ , treat it as a current source


$$I_c(s) = sC V_c(s) - C v_c(0^-)$$

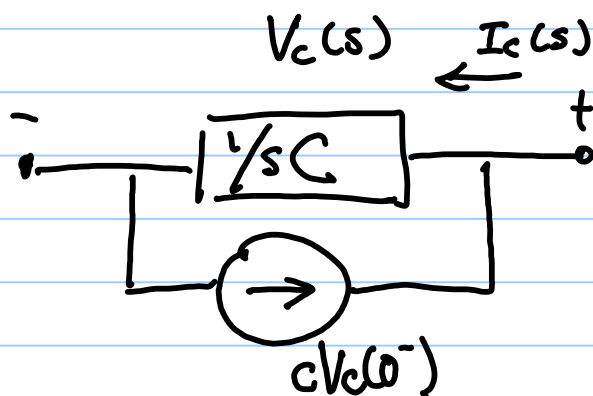


Norton equivalent

$$V_c(s) = \frac{1}{sC} I_c(s) + \frac{1}{s} v_c(0^-)$$

voltage source

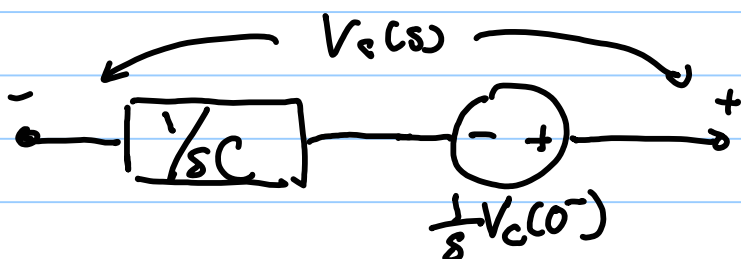

## Inductor

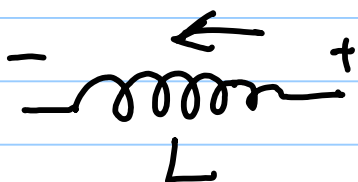

$$V_L(t) = L \frac{d i_L(t)}{dt}$$


$$V_L(s) = L [s I_L(s) - i_L(0^-)]$$

$$= sL I_L(s) - L i_L(0^-)$$


if  $i_L(0) = 0 \Rightarrow V_L(s) = sL I_L(s)$  or  $\frac{V_L(s)}{I_L(s)} = sL$

If not


$$V_L(s) = sL I_L(s) - L i_L(0^-)$$

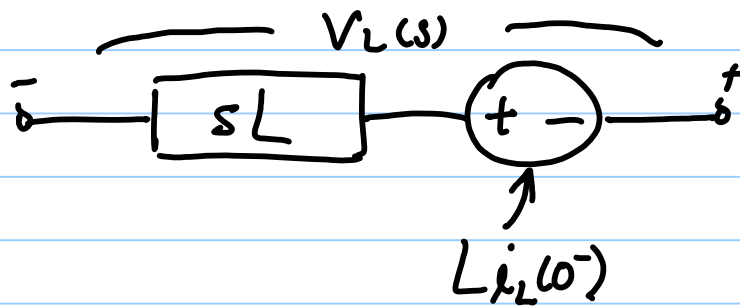
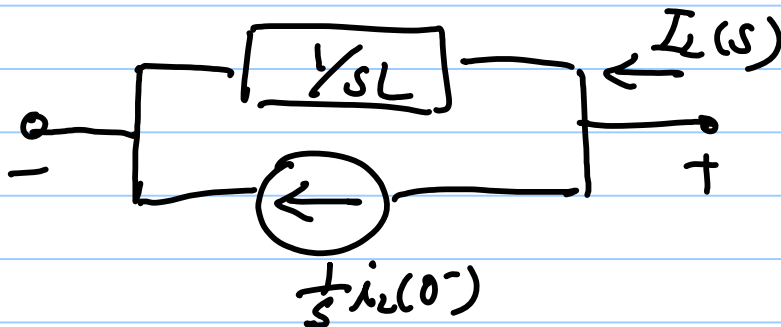
$$I_L(s) = \frac{1}{sL} V_L(s) + \frac{1}{s} i_L(0^-)$$




Example

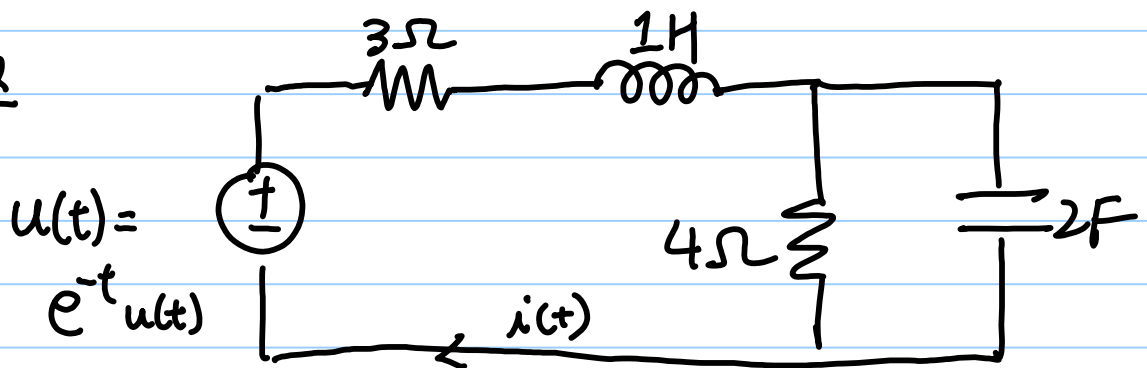


Find  $i(t)$  assume Initial Conditions are zero.

Step 1 - Convert the circuit to s-domain

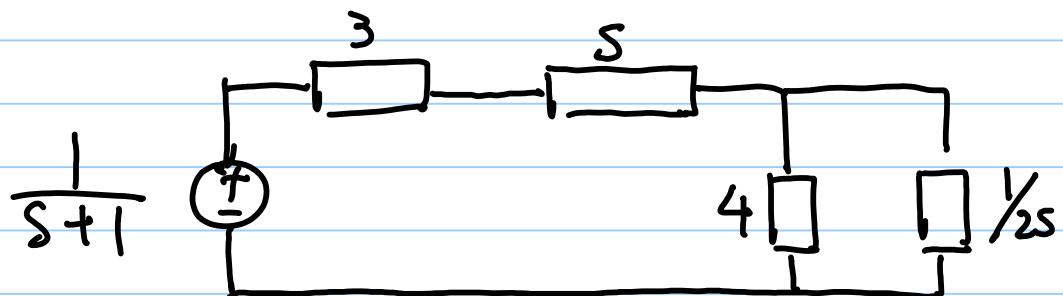

step 2 Treat as a resistive network

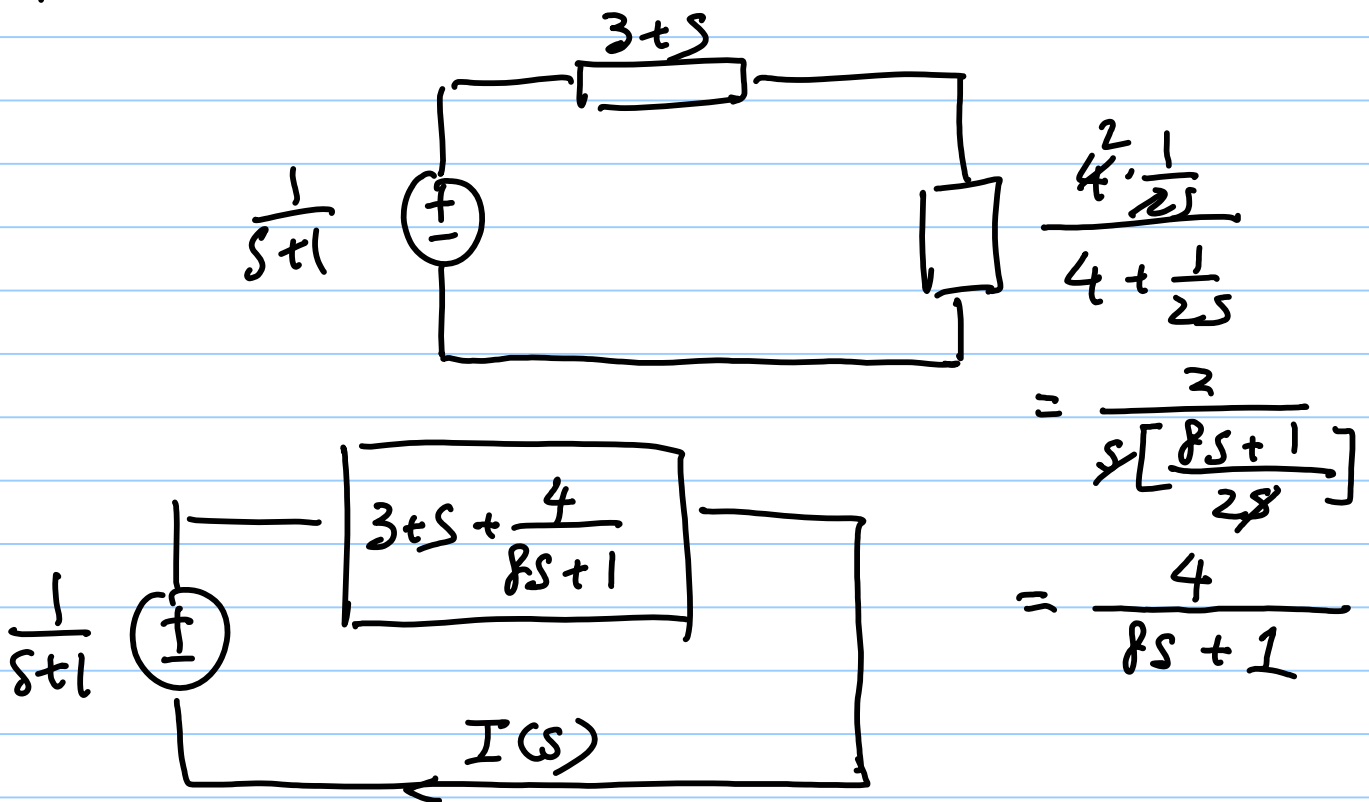

$$I(s) = \frac{\frac{1}{s+1}}{\left(3+s + \frac{4}{8s+1}\right)}$$



Rational function

⇒ will talk about  $\mathcal{L}^{-1}[\ ]$  of that  
in a moment

$$\Rightarrow \mathcal{L}^{-1}[I(s)] = i(t)$$



$$\frac{100}{23} = 4 \frac{8}{23}$$

proper!

$$X(s) = s+1 + \frac{4s}{s^4 + 4s^3 + 5s^2 + 4s + 4}$$

$$\mathcal{L}\left[\frac{dx}{dt}\right] = sX(s) - x(0^-)$$

$$\mathcal{L}^{-1}[1] = \delta(t)$$

$$\mathcal{L}^{-1}[s] = \delta^{(1)}(t)$$

Rarely seen.

2°) Factorize the denominator. (MATLAB)

$$s^4 + 4s^3 + 5s^2 + 4s + 4 = (s+2)^2 (s^2+1) = (s+2)^2 (s+j)(s-j)$$

In matlab  $\Rightarrow$  roots([1 4 5 4 4])

deg=1

3°) Partial Fraction Expansion

$$X(s) = \frac{4s}{(s+2)^2 (s^2+1)} = \frac{A}{s+2} + \frac{B}{(s+2)^2} + \frac{C}{s+j} + \frac{\bar{C}}{s-j}$$

unknown.

Four simple rules:

$$\textcircled{1} \frac{\dots}{\dots (s+a) \dots} \rightarrow \dots + \frac{A}{s+a} + \dots$$

Real #

$$\text{multiplier root } \textcircled{2} \frac{\dots}{\dots (s+a)^n \dots} \rightarrow \dots + \frac{A_1}{s+a} + \frac{A_2}{(s+a)^2} + \dots + \frac{A_n}{(s+a)^n} + \dots$$

$$\textcircled{3} \quad \frac{\dots}{\dots (s+\alpha)(s+\bar{\alpha}) \dots} \rightarrow \dots + \frac{A}{s+\alpha} + \frac{\bar{A}}{s+\bar{\alpha}} + \dots$$

complex conjugates  
 $\swarrow \searrow$   
 $A \quad \bar{A}$

$\uparrow$   
 complex  
 conjugate  $\because$  real coefficients.

$$\textcircled{4} \quad \frac{\dots}{\dots (s+\alpha)^n (s+\bar{\alpha})^n \dots} \rightarrow \dots + \frac{A_1}{s+\alpha} + \frac{A_2}{(s+\alpha)^2} + \dots + \frac{A_n}{(s+\alpha)^n} + \dots$$

$$\dots + \frac{\bar{A}_1}{s+\bar{\alpha}} + \frac{\bar{A}_2}{(s+\bar{\alpha})^2} + \dots + \frac{\bar{A}_n}{(s+\bar{\alpha})^n} + \dots$$

Step 4) Solve for the unknowns in partial fraction

$$X(s) = \frac{4s}{(s+2)^2(s^2+1)} = \frac{A}{s+2} + \frac{B}{(s+2)^2} + \frac{C}{s+j} + \frac{\bar{C}}{s-j}$$

$$\frac{\overset{0}{\parallel} (A+2\text{Re}(C))s^3 + (2A+B+8\text{Re}(C)+2\text{Im}(C))s^2 + \overset{0}{\parallel} \overset{1}{\parallel}}{(s+2)^2(s^2+1)} = \frac{\overset{4}{\parallel} (A+8\text{Re}(C)+8\text{Im}(C))s + (2A+B+8\text{Im}(C)) \overset{0}{\parallel}}{\overset{0}{\parallel}}$$

Heaviside's Theorem :

$$X(s) = \frac{4s}{(s+2)^2(s^2+1)} = \frac{A}{s+2} + \frac{B}{(s+2)^2} + \frac{C}{s+j} + \frac{\bar{C}}{s-j}$$

$$X(s)(s+2)^2 = A(s+2) + B + \frac{C(s+2)^2}{s+j} + \frac{\bar{C}(s+2)^2}{s-j}$$

$$\underset{\parallel}{\frac{4s}{(s^2+1)}}$$