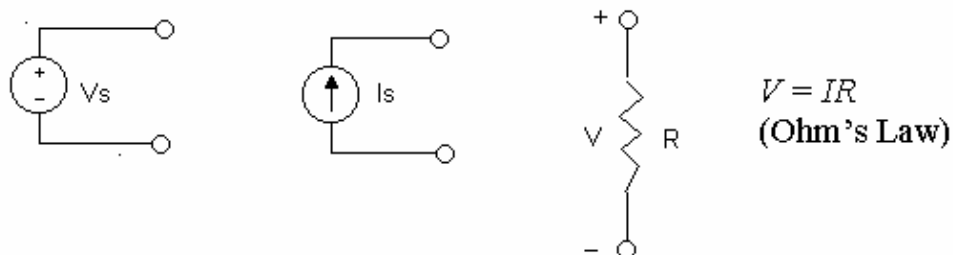


# Applications of the Laplace Transform


## Application in Circuit Analysis

### 1. Review of Resistive Network


#### 1) Elements




#### 2) Superposition

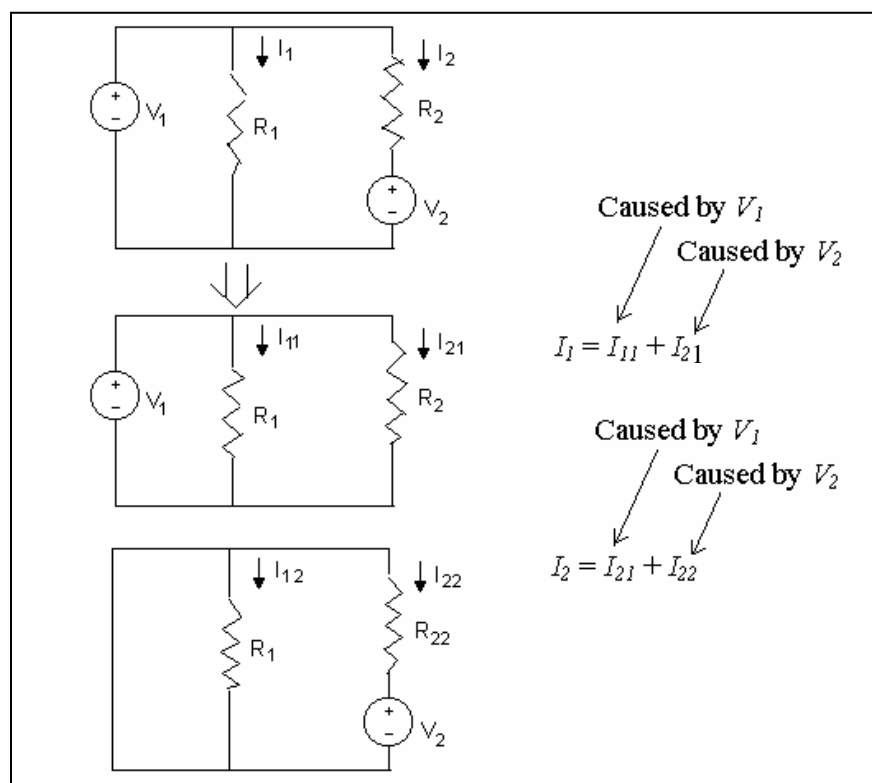

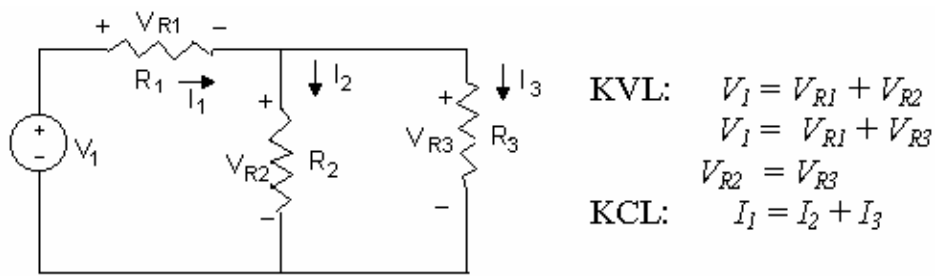
3) KVL and KCL – Select a node for ground. Watch out for signs!



4) Equivalent Circuits

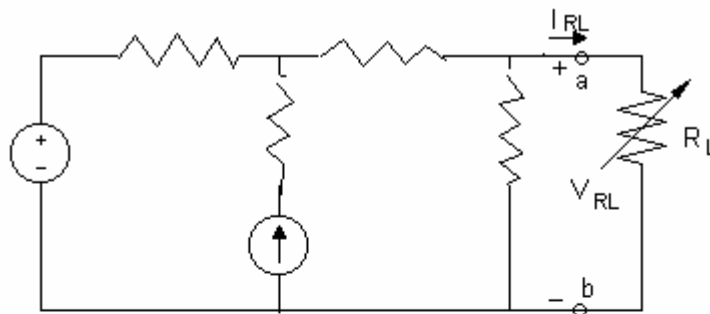


Thevenin  
Equivalent  
Circuit

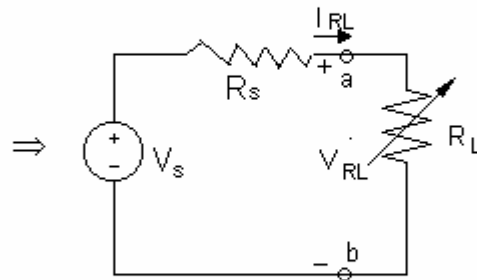


$V_s = V_{OC} = \text{Open Circuit Voltage}$   
 $R_s = \text{Equivalent Resistance}$

Norton  
Equivalent  
Circuit

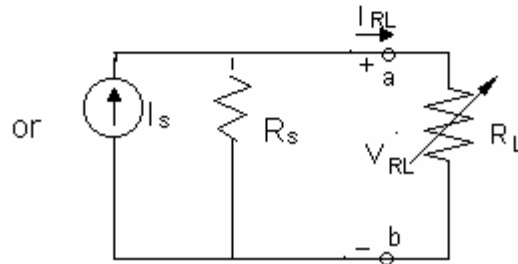

$I_s = I_{SC} = \text{Short Circuit Current}$   
 $R_s = \text{Same as before}$

5) Nodal Analysis and Mesh Analysis

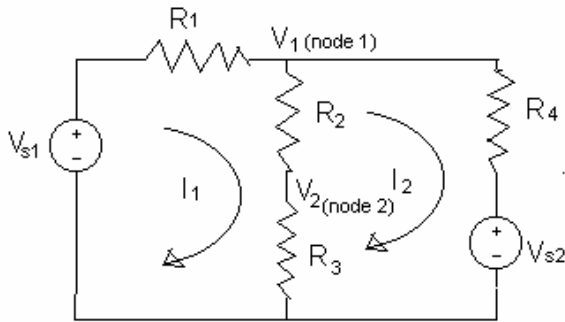

**Nodal Analysis** (Use KCL)

$$\begin{cases} \frac{V_{s1} - V_1}{R_1} + \frac{V_2 - V_1}{R_2} + \frac{V_{s2} - V_1}{R_4} = 0 \\ \frac{V_1 - V_2}{R_2} + \frac{0 - V_2}{R_3} = 0 \end{cases}$$

Solve for  $V_1$  and  $V_2$  and then calculate other currents and voltages.


**Mesh analysis** (use KVL)

$$\begin{cases} V_{s1} = R_1 I_1 + R_2 (I_1 - I_2) + R_3 (I_1 - I_2) \\ V_{s1} = R_1 I_1 + R_4 I_2 + V_{s2} \end{cases}$$

Solve for  $I_1$  and  $I_2$ .

2. Characteristics of Dynamic Networks


1) Inductor

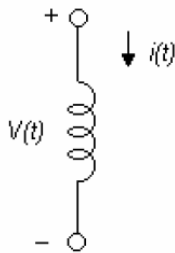

$$v_L(t) = L \frac{d}{dt} i_L(t)$$

$$\text{or } i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$


2) Capacitor

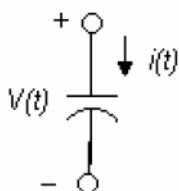

$$i_C(t) = C \frac{d}{dt} v_C(t)$$

$$\text{or } v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

### 3) Operation Amplifier

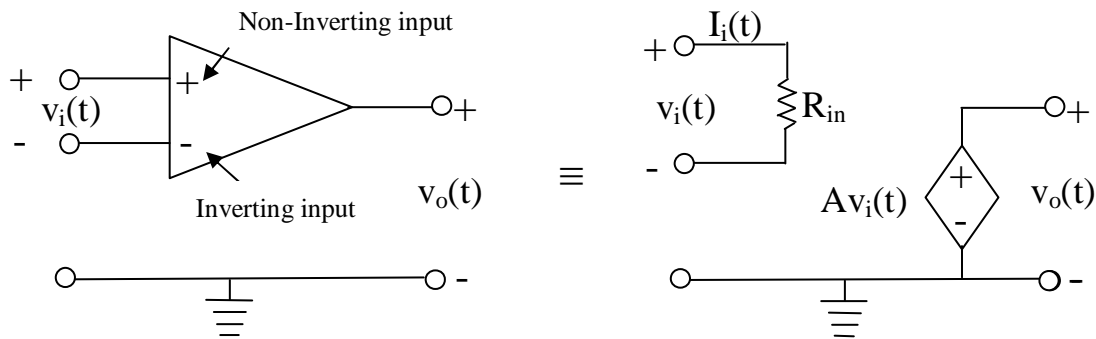


A general op-amp model is described above.

In practice, the input resistance,  $R_{in}$ , is very large ( $> 10^{12} \Omega$ ) and the gain,  $A$ , is very large ( $> 10^5$ ). Thus, we will use the ideal model in the analysis:

1. Input current  $I_i(t) = 0$  (due to the large input impedance)
2. Input voltage difference  $v_i(t) = 0$  and output voltage  $v_o(t)$  is dictated by external circuit (due to the large gain)

Example:

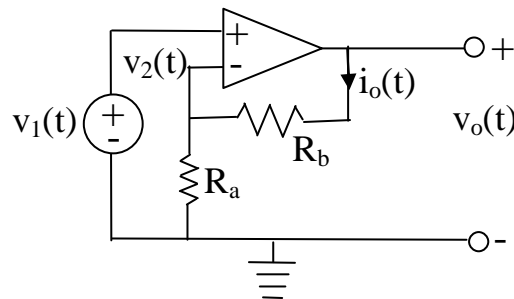

Based on the ideal op-amp model,

$$v_2(t) = v_1(t) \tag{1}$$

Also, as the op-amp does not have any input current, applying KCL at the inverting port, we have


$$\begin{aligned} v_2(t)/R_a &= (v_o(t)-v_2(t))/R_b \\ v_o(t)/v_2(t) &= 1+R_b/R_a \\ v_o(t)/v_1(t) &= 1+R_b/R_a \end{aligned}$$

Plug in (1), we have

This circuit is called *Non-Inverting Amplifier*.

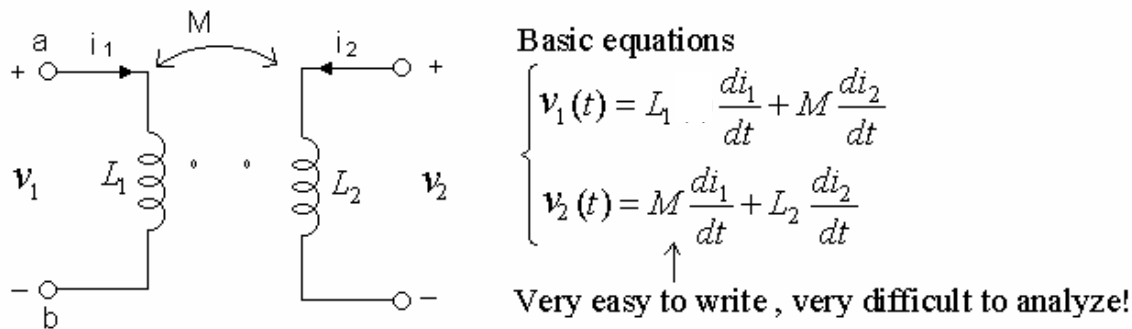4) Mutual Inductor – used in transformer.

Two separate circuits with coupling currents.




Make sure both  $i_1$  and  $i_2$  point either away or toward the polarity marks to make the mutual inductance  $M$  positive.


To link the two circuits together, introduce a combined current term ( $i_1+i_2$ ):

$$\begin{aligned} v_1(t) &= L_1 \frac{di_1}{dt} - M \frac{di_1}{dt} + M \frac{di_1}{dt} + M \frac{di_2}{dt} \\ &= (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt}(i_1 + i_2) \\ v_2(t) &= M \frac{di_1}{dt} + M \frac{di_2}{dt} + L_2 \frac{di_2}{dt} - M \frac{di_2}{dt} \\ &= M \frac{d}{dt}(i_1 + i_2) + (L_2 - M) \frac{di_2}{dt} \end{aligned}$$

Equivalent circuit:

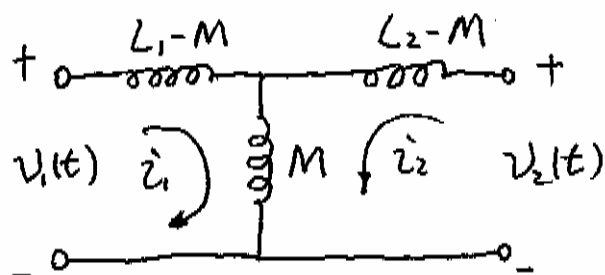

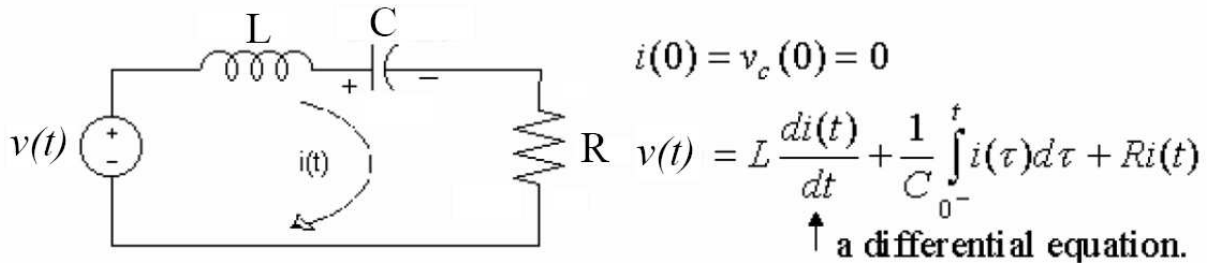Example : Apply mesh analysis to the following circuit



Using Laplace Transform

$$\begin{aligned} V(s) &= V_L(s) + V_C(s) + V_R(s) \\ &= L(sI(s) - i(0^-)) + \frac{1}{C} \left[ \frac{I(s)}{s} + \frac{v_c(0)}{s} \right] + RI(s) \\ &= (Ls)I(s) + \frac{1}{Cs} I(s) + RI(s) \end{aligned}$$

Define ‘Generalized Resistors’ (Impedances)

$$Z_L(s) = Ls \Rightarrow V_L(s) = I(s)Z_L(s)$$

$$Z_C(s) = \frac{1}{Cs} \Rightarrow V_C(s) = I(s)Z_C(s)$$

Both capacitor and inductor behave exactly like a resistor!

$$\Rightarrow V_s(s) = Z_L(s)I(s) + Z_C(s)I(s) + RI(s)$$

$$\Rightarrow I(s) = \frac{V_s(s)}{Z_L(s) + Z_C(s) + R}$$


Everything we know about resistive network can be applied to dynamic network in Laplace domain:

- Generalized Ohms Law
- superposition
- KVL and KCL
- Equivalent circuit
- Nodal analysis and mesh analysis

3. Laplace transform models of circuit elements.

What if the initial conditions are not zero?

1) Capacitor

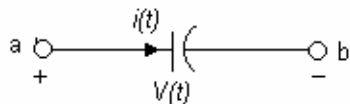


$$i(t) = C \frac{dv(t)}{dt}$$

$$I(s) = CsV(s) - Cv(0^-)$$

$$V(s) = \frac{1}{Cs}I(s) + \frac{1}{s}v(0^-)$$


define  $Z_C(s) = \frac{1}{Cs}$
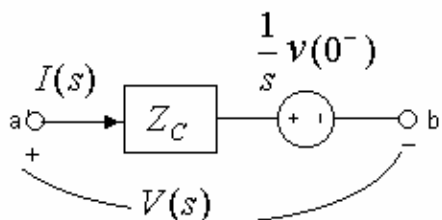
$$V(s) = Z_C(s)I(s) + \frac{1}{s}v(0^-)$$




⇒ model: an impedance ('generalized resistor') and a voltage source in series.

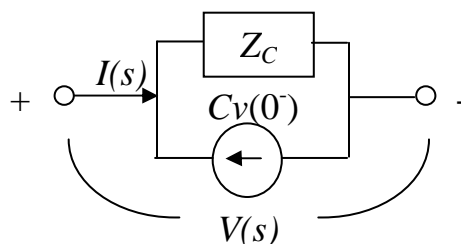Alternatively, you can also represent it as an impedance and a parallel current source (Norton equivalent circuit)



**BE VERY CAREFUL ABOUT THE POLARITY OF VOLTAGE SOURCE AND THE DIRECTION OF CURRENT SOURCE!!**

2) Inductor

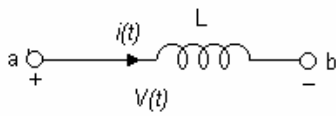


$$V(t) = L \frac{di(t)}{dt}$$

$$V(s) = LsI(s) - Li(0^-)$$

'Generalized resistor' (Impedance)


$$Z_L(s) = Ls \quad \text{and}$$

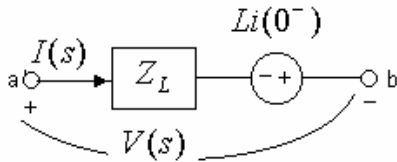a negative voltage source  $Li(0^-)$  in series.




Can we obtain  $V(s) = LsI(s) - Li(0^-)$   
From this circuit models?  
Yes!

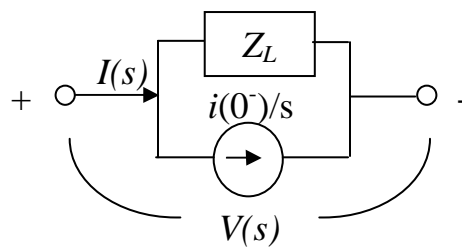Alternatively, you can also represent it as an impedance and a parallel current source (Norton equivalent circuit)




3) Resistor  $V(s) = RI(s)$

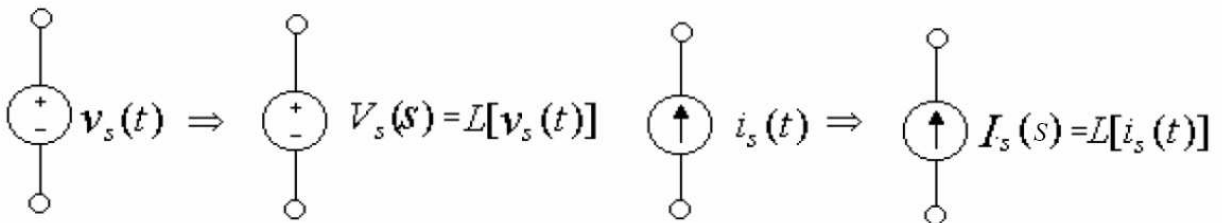4) Voltage and Current Sources (Don't forget to apply Laplace Transform on them)




5) Op-Amp : same ideal model assumption


6) Mutual Inductance (Transformers)

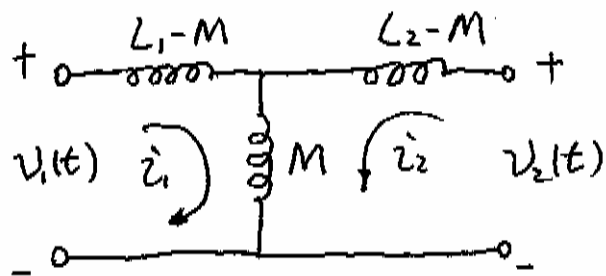

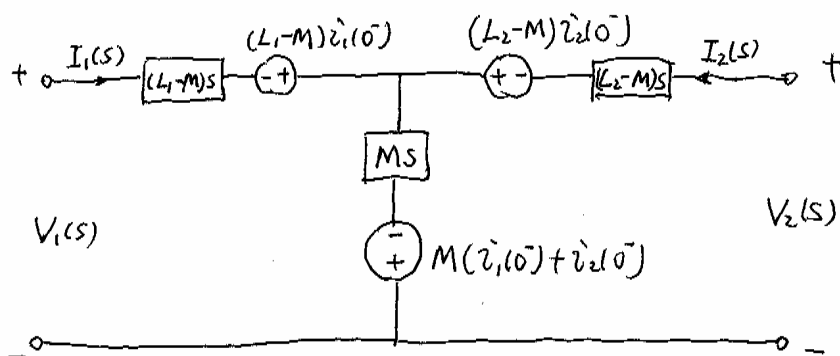⇓ Laplace transform model: Obtain it by using inductance model




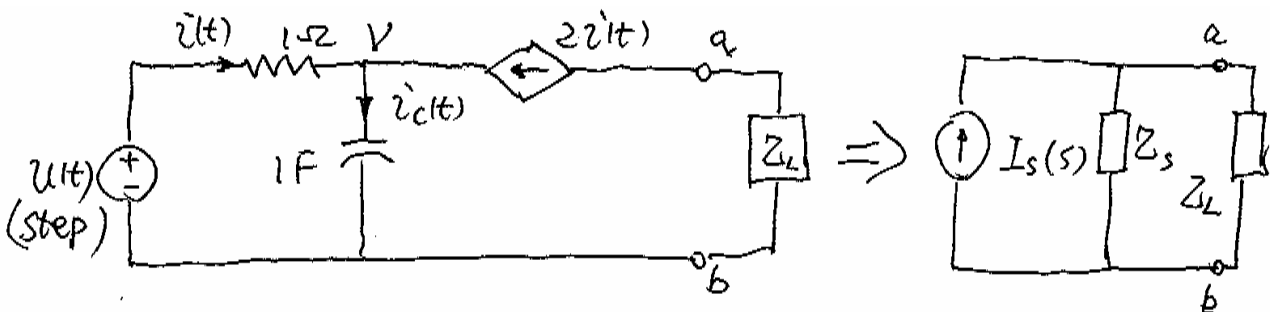Example: Find Complex Norton Equivalent circuit given  $v_c(0^-) = 0$



Solution

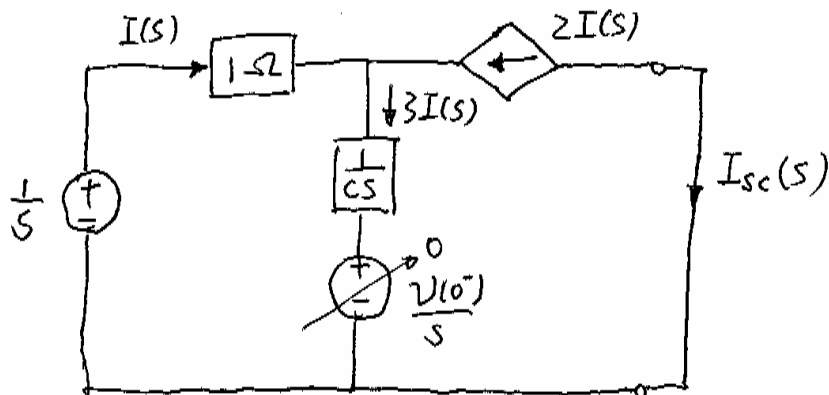1) Compute the Short-Circuit Current  $I_s(s) = I_{sc}$



Straightforward to see:  $I_s(s) = -2I(s)$

To compute  $I(s)$ , apply mesh analysis on the left loop:

$$\frac{1}{s} = I(s) \times 1 \Omega + 3I(s) \frac{1}{s} = \left(1 + \frac{3}{s}\right) I(s) = \frac{s+3}{s} I(s)$$


$$\Rightarrow I(s) = \frac{1}{s+3}$$

$$\Rightarrow I_s(s) = -2I(s) = -\frac{2}{s+3}$$

No need to do inverse Laplace transform as the equivalent circuit is in the s-domain.

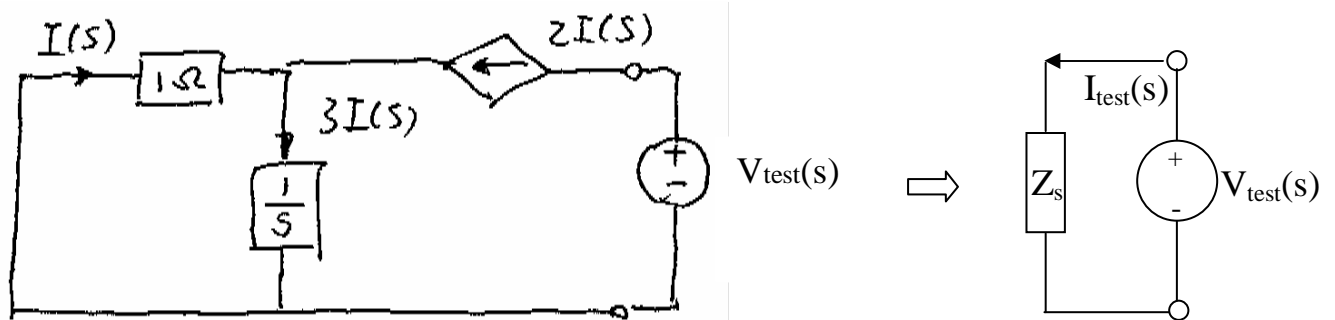2) Find the equivalent impedance  $Z_s$

Normally, we can just kill all the independent sources and combine the impedances (using resistive combination rules). However, as there is a dependent source, we need to drive it with a test voltage:



$$Z_s = \frac{V_{test}(s)}{I_{test}(s)} = \frac{V_{test}(s)}{2I(s)}$$


Mesh analysis on the left loop:

$$I(s) \times 1\Omega + \frac{3I(s)}{s} = 0$$

$$\Rightarrow (1\Omega)I(s) = -\left(\frac{3}{s}\right)I(s)$$


$$\Rightarrow I(s) = 0$$

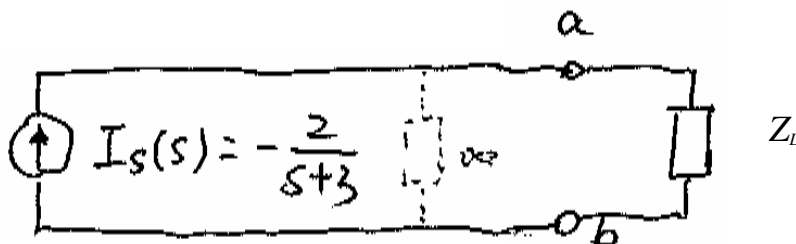So we got an interesting result:  $Z_s = \frac{V_{test}(s)}{0} = \infty \Rightarrow$  OPEN CIRCUIT




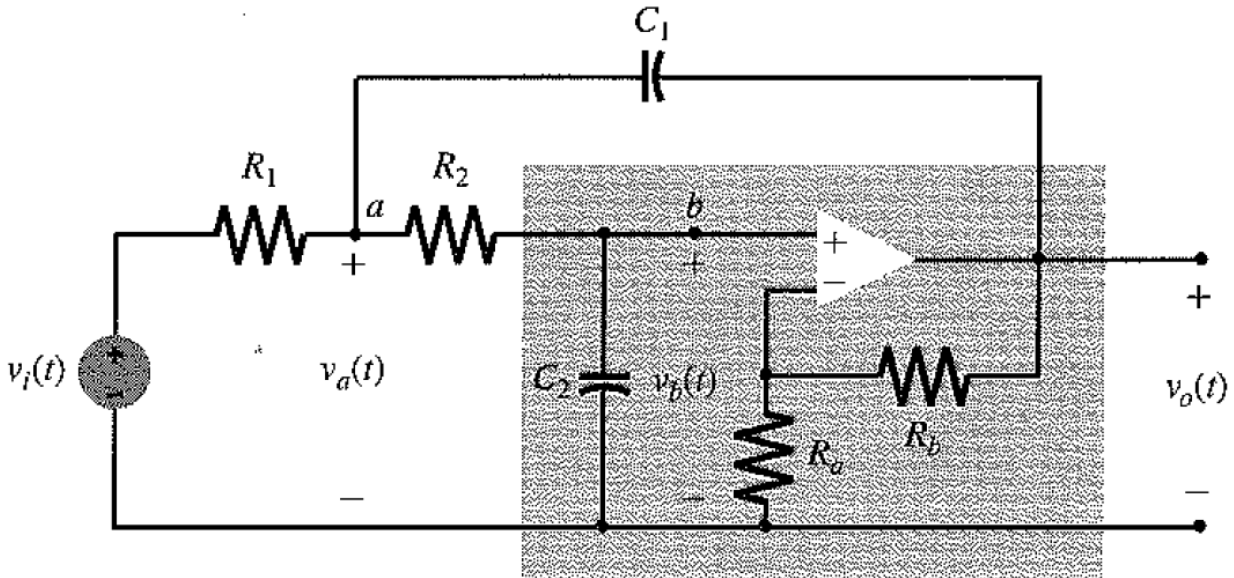Example: Find the transfer function  $H(s) = V_o(s)/V_i(s)$  of the following circuit. Assume all initial conditions are zero.

This is called the Sallen-Key circuit, which we will see again in filter design.



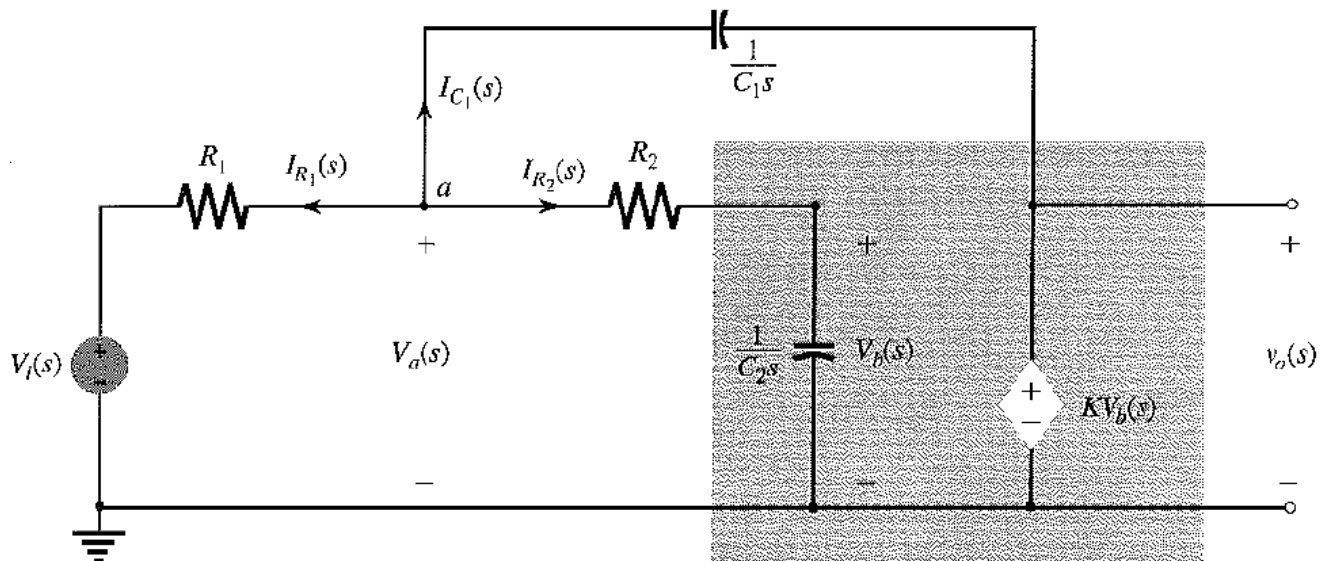Rewrite everything in Laplace domain, we have



We recognize the op-amp configuration as a non-inverting amplifier, so we have

$$K = 1 + \frac{R_b}{R_a}$$

To find  $V_o$ , we need  $V_b$  which depends on  $V_a$ .

All other nodal voltages are known. Thus, we need two nodal equations:

Applying KCL at node a, we have:

$$\begin{aligned} \frac{V_a - V_i}{R_1} + \frac{V_a - V_b}{R_2} + \frac{V_a - KV_b}{1/C_1 s} &= 0 \\ \Rightarrow \left( \frac{1}{R_1} + \frac{1}{R_2} + C_1 s \right) V_a - \left( \frac{1}{R_2} + KC_1 s \right) V_b &= \frac{1}{R_1} V_i \end{aligned} \quad (1)$$

Applying KCL at node b, we have:

$$\begin{aligned} \frac{V_b - V_a}{R_2} + C_2 s V_b &= 0 \\ \Rightarrow -\frac{1}{R_2} V_a + \left( \frac{1}{R_2} + KC_1 s \right) V_b &= 0 \end{aligned} \quad (2)$$

Combining equations (1) and (2) by eliminating  $V_a$ , we get:

$$\frac{V_b}{V_i} = \frac{1}{R_1 R_2 C_1 C_2 s^2 + [R_2 C_2 + R_1 C_2 + R_1 C_1 (1 - K)] s + 1}$$

Since  $V_o = KV_b$ , we have

$$\frac{V_o}{V_i} = \frac{K}{R_1 R_2 C_1 C_2 s^2 + [R_2 C_2 + R_1 C_2 + R_1 C_1 (1 - K)] s + 1}$$

where  $K = 1 + \frac{R_b}{R_a}$